 


Delay


- Gate delay $T_g = f(\text{input slew, output load})$
 - The higher input slew, load, the higher gate delay
 - Load is C_{equ} = equivalent capacitance of the parasitics and cell loads
 - Improve gate delay:
 - Optimize C_{in} of next stages by using small load cells while preserving timing
 - Matching C_{equ} and driver's strength -> save power
 - Using low V_t type cells ->
 - High leakage but possible lower short circuit power (internal cell power)
 - Only for critical paths
- Wire Delay:
 - Simple formula: Elmore delay = $T_{pd} = \sum R(n-i)C_i$
 - Improve wire delay:
 - Reducing R and/or C :
 - For long wires, resistance dominates -> reduce R first by increasing wire width
 - Too long wires -> buffer insertion -> cut total delay to half or even $\frac{1}{3}$, $\frac{1}{4}$.

Optimize long wire delay by buffer insertion

Total delay
($T_g + T_w$)



CLOCK SKEW

 


$$Td2 = Tclk1 + Tck2q + Tp1$$

$$Tclk2 = Tclk + skew2$$


$$Tclk3 = Tclk + skew2 - dskew, dskew > 0 \rightarrow \text{CLK3 is earlier than CLK2}$$

$$Td3 = Tclk + skew2 + Tck2q + Tp2$$

 The clock skew between CLK2 and CLK3 makes the path P2 more critical



CLOCK SKEW

 

- What causes clock skew?
 - CTS
- Consequences of clock skew
 - Reduced performance
 - Failed functional
- How to reduce clock skew?
 - Clock spines
 - Clock mesh
 - Htree
 - ...

Power

Total Power = P_{switch} + $P_{\text{short_circuit}}$ + P_{leakage}

- $P_{\text{switch}} = aCV^2f$ ($C = C_{\text{equ}}$ of load), a = switching activity
 -
- $P_{\text{short_circuit}} \sim \text{slew, frequency}$
 - Use strong cells (large width or low V_t)
- P_{leakage} :
 - Use weak cells (min width or high V_t)

Depending upon which application that which type of power will dominate -> corresponding optimization

Signal Integrity

How to fix:

- Driver optimization: driver strength needs to match load, not too strong neither too weak.
- Buffer insertion: For long wire, even very big driver is not enough
- Crosstalk:
 - a. Increase space to reduce coupling cap
 - b. Add shielding for critical nets
 - c. Increase strength of the drivers of the victim nets
 - d. Decrease strength of the drivers of the aggressor nets
- Using NDR (Non Default Rule)

Questions

1. Clock skew:
 - a. What is clock skew? Is it important? Why?
 - b. What causes clock skew? How to reduce the clock skew?
 - c. Is global clock skew or local clock skew important? Why?
2. Why is transition time measured from 10 to 90%?
3. Does improving gate delay also reduce wire delay?
4. What is the plus/minus of increasing the transistor width?
5. What are the components of power dissipation in a design? Which one is the most important?
6. What is crosstalk? When does crosstalk become significant? How to avoid/reduce crosstalk?