

LSI LOGIC DESIGN

CHAPTER 2

Logic Elements and Electronic Signal on Silicon


APRIL 28, 2020

PHAM TUONG HAI

QUALITY ASSESSMENT & TRAINING DEPARTMENT

RENESAS DESIGN VIETNAM CO., LTD.

RENESAS ELECTRONICS CORPORATION

 

CHAPTER 2. Logic Elements and Electronic Signal on Silicon



- 2.1. Digital Logic and CMOS Circuit.
- 2.2. Logic Gate on Silicon.
- 2.3. Electronic Signal Propagation on Silicon.
- 2.4. Problem with Electronic Signal.

2.1 Digital Logic and CMOS Circuit

Devices Implemented in LSI



○ MOS Transistor

  Broadly used owing to the properties of high-speed, low-voltage, and high-integration.




○ Bipolar Transistor

  Used in RF and analog applications owing to its high-drive-ability.



○ Other devices

Diode, resistors, capacitors etc.

 

MOS: Metal Oxide Semiconductor

What is Semiconductor?

A semiconductor is a material that behaves between a conductor and an insulator.

At room temperature, semiconductor has higher electric conductivity than an insulator, but lower than a conductor.

At very low temperatures, pure or intrinsic semiconductors behave like insulators.


At higher temperatures or under light, pure or intrinsic semiconductors can become conductive.

The addition of impurities to a pure semiconductor can also increase its conductivity.

What is Semiconductor?

 - a) **Conductor** (**Cu, Al**) electron free from atomic bound
- b) **Semiconductor** (**Si, Ge, GaAs**) electron loosely bounded to atom
- c) **Insulator** (**SiO₂, SiN**) electron tightly bounded to atom

Materials are grouped by 3 types in electrical resistivity



Intrinsic and Extrinsic Semiconductor

Intrinsic semiconductor

A perfect semiconductor which has no impurities


Its characteristics comes from the semiconductor itself

Extrinsic semiconductor

A semiconductor to which impurity is doped

Some part of its characteristics comes from the doped impurity

Group	III	IV	V
	5	6	7
	B	C	N
	13	14	15
	Al	Si	P
	31	32	33
	Ga	Ge	As

 


P-type Silicon - Acceptor

It is very easy for an electron from a nearby **Silicon** to **Silicon** bond to fall into this hole and effectively move the hole away from the **Boron** atom

Since the **Boron** atom will accept an electron, **Boron** and the other elements of Group III (**B**, **Ga**) are referred to as **acceptors**

 Silicon with acceptor is called as **P-type Silicon**, since “positive” holes are generated and contribute a current flow




N-type Silicon - Donor

If a Group V atom, such as **Phosphorus**, is introduced into the **Silicon** lattice, it will have an extra electron which may easily break away, becoming a conduction electron

The **Phosphorus** is referred to a **donor**, since it donates an electron to the conduction band.

Other donor is **As**

 Silicon with donor is called as **N-type Silicon**, since “negative” electrons are generated and contribute the current flow




Properties of Silicon and Silicon Oxide

TABLE 2.1 Physical Properties of Si and SiO₂ at Room Temperature (300 K)


Property	Si	SiO ₂
Atomic/molecular weight	28.09	60.08
Atoms or molecules/cm ³	5.0×10^{22}	2.3×10^{22}
Density (g/cm ³)	2.33	2.27
Crystal structure	Diamond	Amorphous
Lattice constant (Å)	5.43	—
Energy gap (eV)	<u>1.12</u>	8–9
Dielectric constant	11.7	<u>3.9</u>
Intrinsic carrier concentration (cm ⁻³)	<u>1.4×10^{10}</u>	—
Carrier mobility (cm ² /V-s)	<u>Electron: 1430</u>	—
	<u>Hole: 470</u>	—
Effective density of states (cm ⁻³)	Conduction band, N_c : 3.2×10^{19}	—
	Valence band, N_v : 1.8×10^{19}	—
Breakdown field (V/cm)	3×10^5	$>10^7$
Melting point (°C)	1415	1600–1700
Thermal conductivity (W/cm-°C)	1.5	0.014
Specific heat (J/g-°C)	0.7	1.0
Thermal diffusivity (cm ² /s)	0.9	0.006
Thermal expansion coefficient (°C ⁻¹)	2.5×10^{-6}	0.5×10^{-6}

MOS Capacitor

 


** actual metal or heavily doped polysilicon*

Behavior of MOS Capacitor

 


MOSFET

*** Focusing on n-channel transistor ***

 

 N+: heavily doped silicon
= low resistive electrode




Channel

L: channel length
W: channel width
FET: Field Effect Transistor


Operation of N-channel MOSFET (1)

- Gate characteristics

 


Sub-threshold region ($0 \leq V_g \leq V_{th}$)

$I_d = 0$ (nearly)

 


Operation of N-channel MOSFET (2)

- Gate characteristics


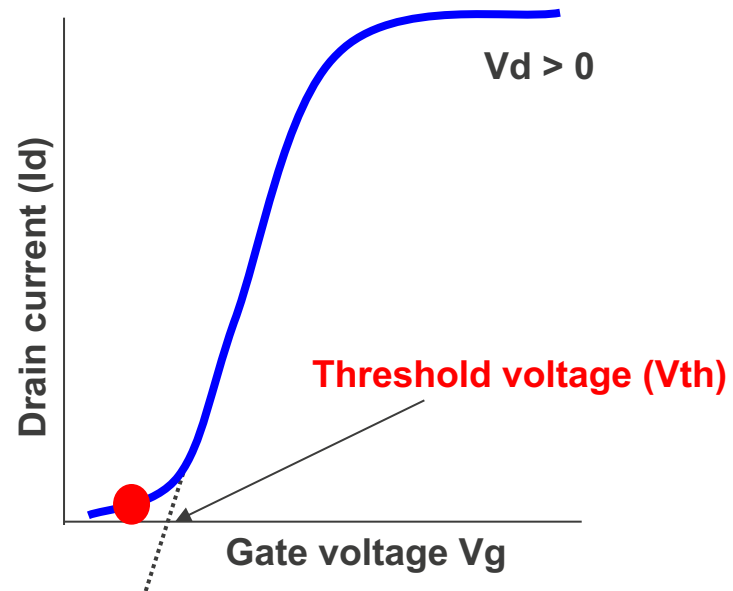


 When $V_g < V_{th}$, the electric current is called **sub-threshold current**. This is one of the leakage currents.





Operation of N-channel MOSFET (3)

- Gate characteristics

  



Operation of N-channel MOSFET (4)

- Gate characteristics

  



Operation of N-channel MOSFET (5)

- Gate characteristics

 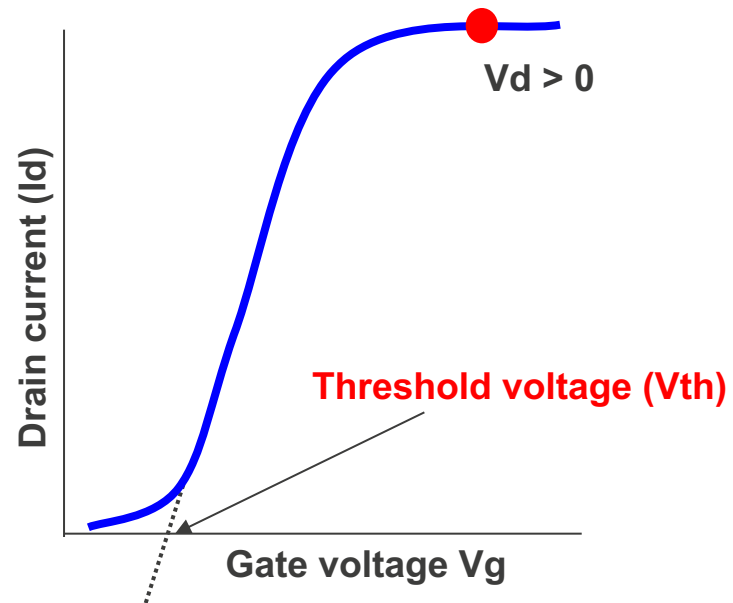

Operation of N-channel MOSFET (6)



▪ Drain characteristics

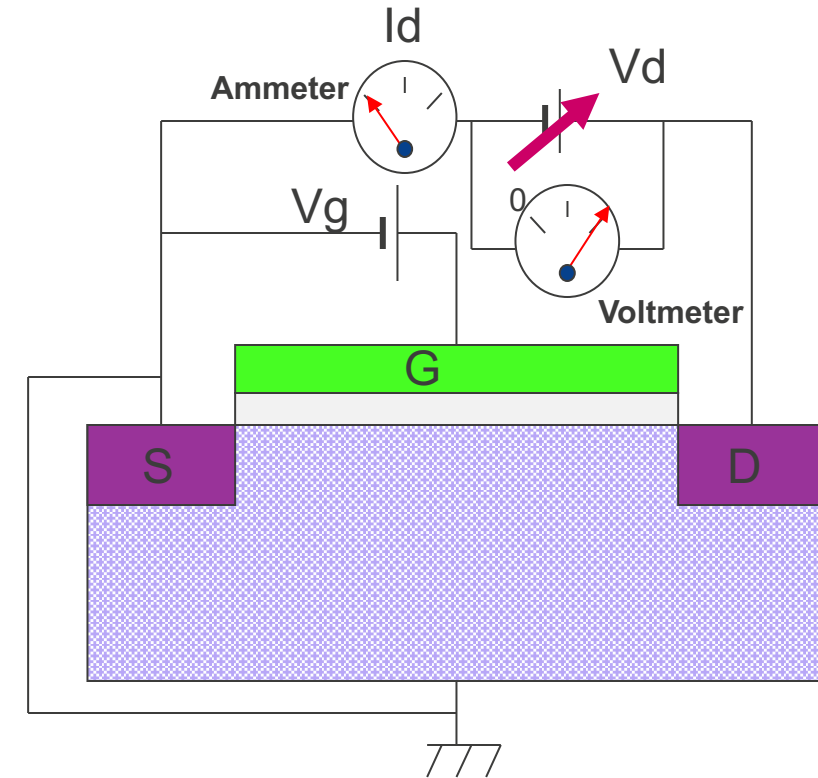 

Even if $V_d > 0$, there is no current (except leakage) when $V_g < V_{th}$.

Operation of N-channel MOSFET (7)



▪ Drain characteristics

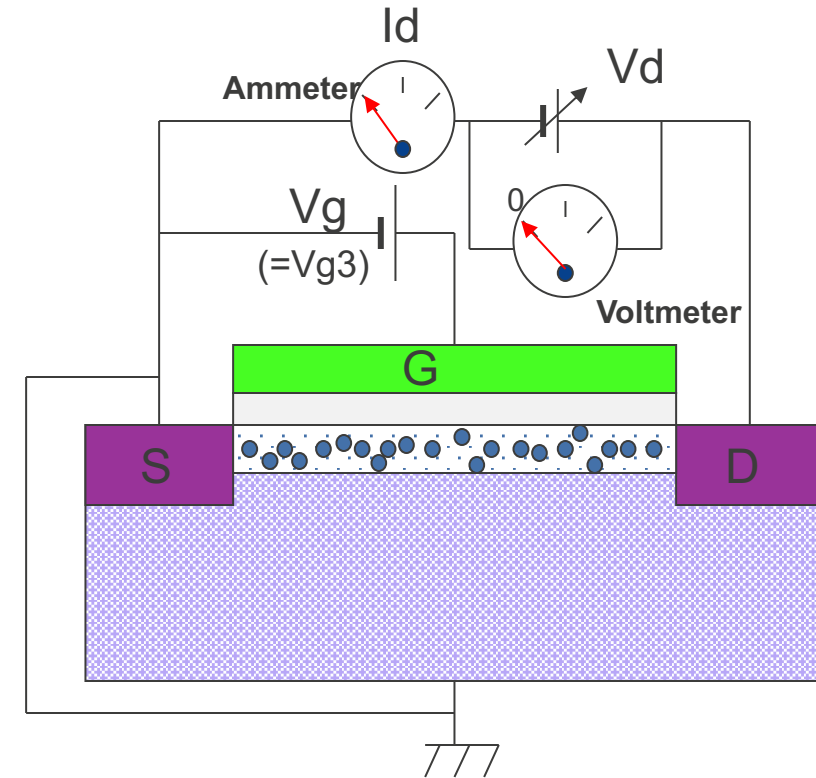 

Apply $V_g = V_{g3}$, and watch what happens.



Operation of N-channel MOSFET (8)

▪ Drain characteristics

  



Operation of N-channel MOSFET (9)

▪ Drain characteristics

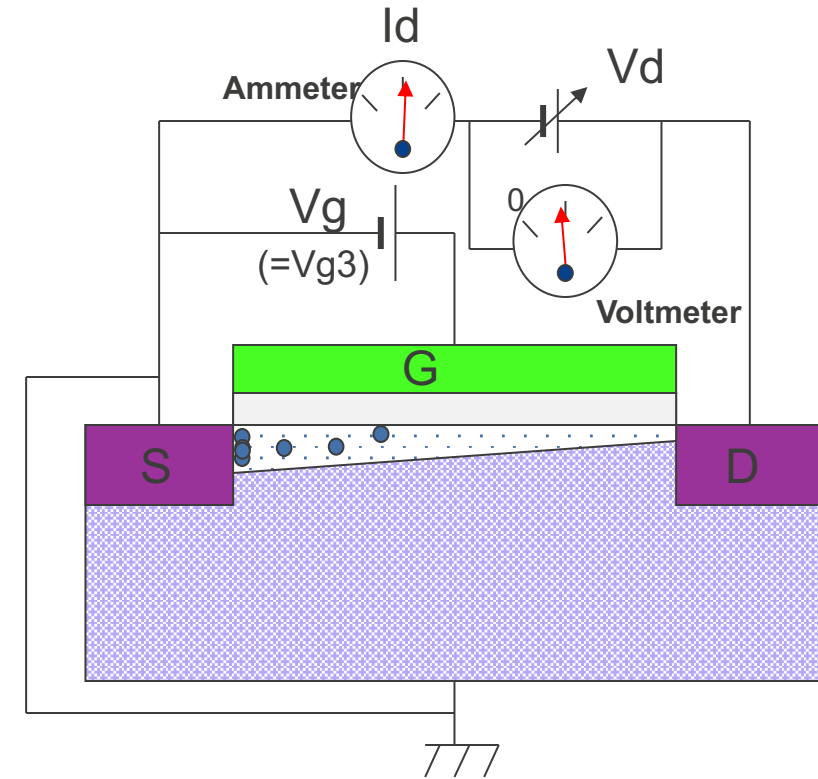 

Operation of N-channel MOSFET (10)



▪ Drain characteristics

  

When $V_d = V_g - V_{th}$, it is called “pinch-off point”.

Operation of N-channel MOSFET (11)

▪ Drain characteristics

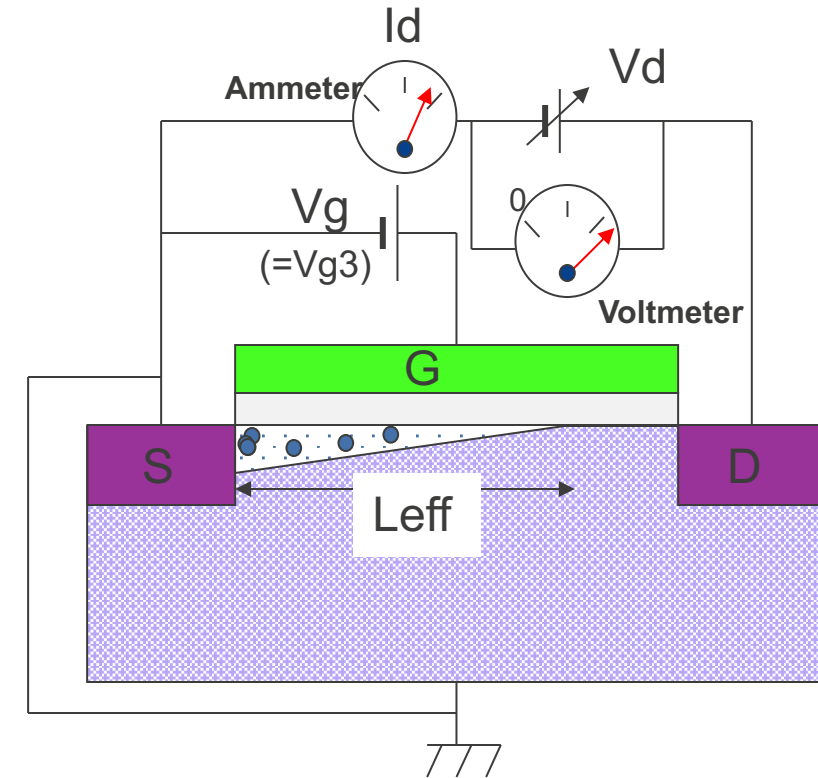 

After pinch-off, the current **becomes constant**.
Electrons are attracted by drain field and flow through the depletion region.


Current characteristics of MOSFET (Summary)

<Fundamental Formula of drain current>

$$I_d = \begin{cases} \beta_n \{V_d(V_g - V_{thn}) - V_d^2/2\} & \text{(Linear region)} \\ & 0 \leq V_d \leq V_g - V_{thn} \\ \beta_n (V_g - V_{thn})^2 / 2 & \text{(Saturation region)} \\ & V_d > V_g - V_{thn} \end{cases}$$

$\beta_n = \mu C_{ox} W/L$
 μ : Electron Mobility
 C_{ox} : Gate capacitance per unit area
 W : Gate width
 L : Gate length
 V_{thn} : Threshold voltage of NMOS
(gate voltage required to switch ON transistor)

<Characteristics of drain current>

 


Drain current at $V_g = V_d = V_{dd}$
is called as

Saturation Conditions:


$$V_{gs} - V_{th} > 0$$

$$V_{ds} > V_{gs} - V_{th}$$

Operations of nMOS Transistor

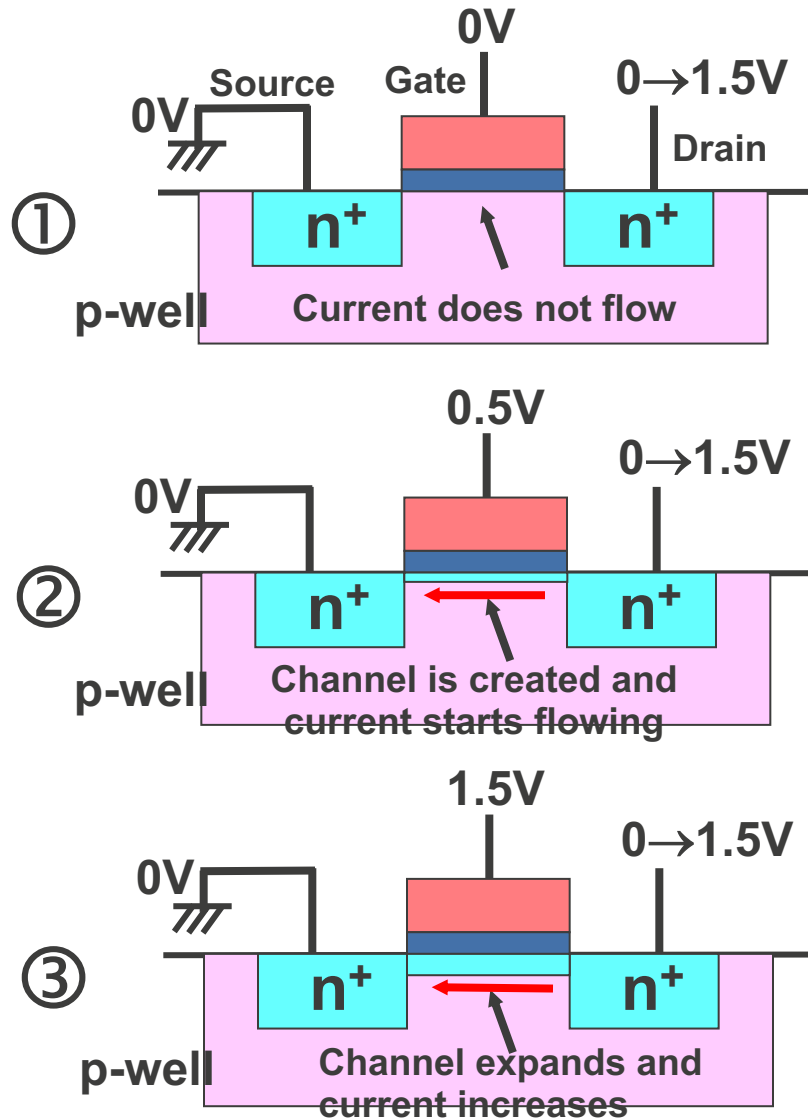

<Characteristics of drain current >

 




<Formula of drain current>

$$I_{ds} = \begin{cases} \beta_n \{V_d \cdot (V_g - V_{thn}) - V_d^2/2\} & (\text{when } 0 \leq V_d \leq V_g - V_{thn}) \\ \beta_n (V_{gs} - V_{thn})^2/2 & (\text{when } V_d > V_g - V_{thn}) \end{cases}$$


β_n : proportionality coefficient

V_{thn} : threshold voltage (gate voltage required to switch ON transistor)

Operations of pMOS Transistor

   

<Current characteristics>

 


<Formula of current>

$$I_{ds} = \begin{cases} -\beta_p \{V_d \cdot (V_g - V_{thp}) - V_d^2/2\} & (\text{when } V_g - V_{thp} \leq V_d \leq 0) \\ -\beta_p (V_{gs} - V_{thp})^2/2 & (\text{when } V_{ds} < V_{gs} - V_{thp}) \end{cases}$$

β_p : proportionality coefficient

V_{thp} : threshold voltage (gate voltage required to switch ON transistor)

Structure of CMOS Transistor

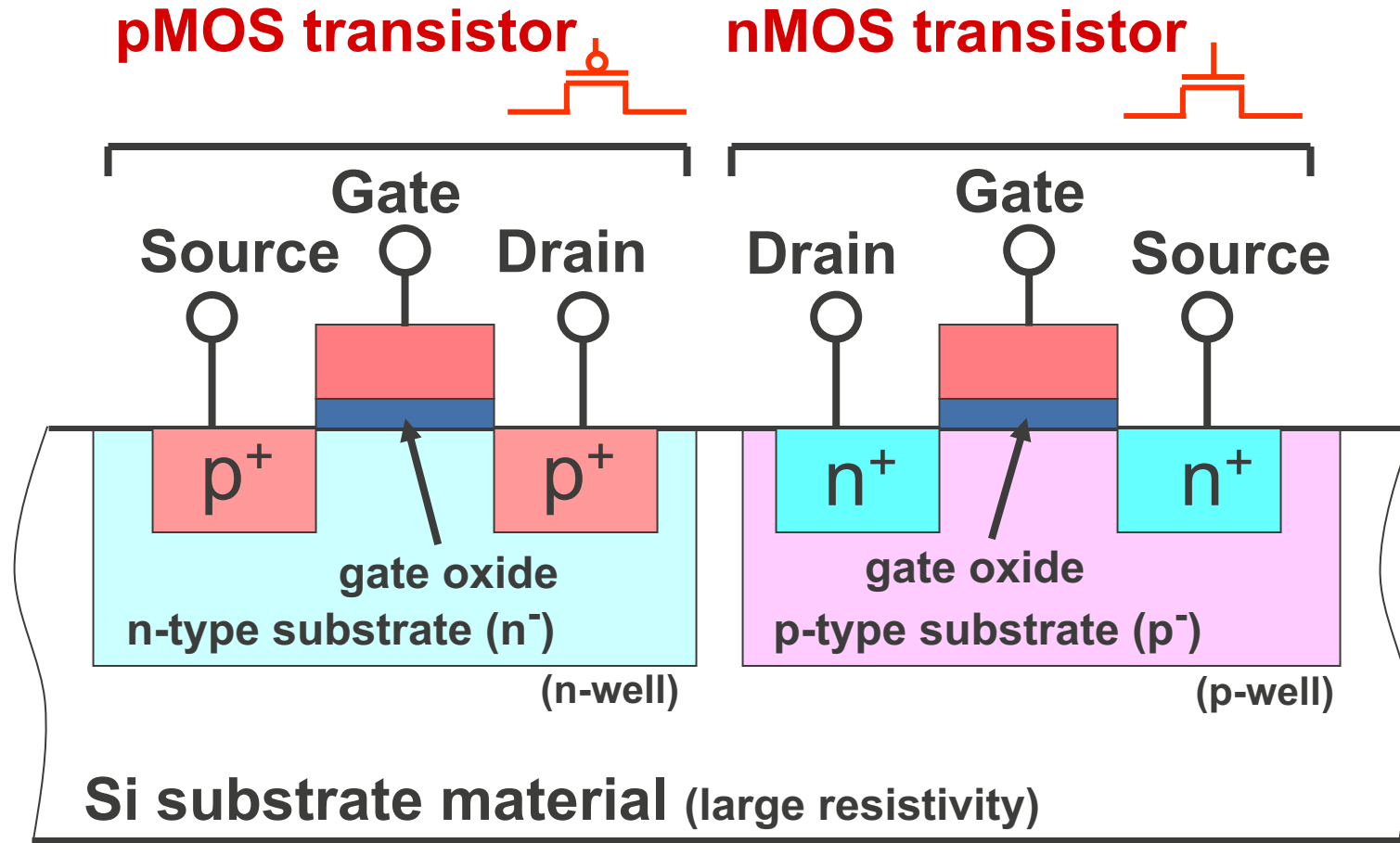


MOS: Metal-Oxide Semiconductor
CMOS: Complementally MOS


2.2 Logic Gate on Silicon

Inverter

<CMOS inverter Structure >

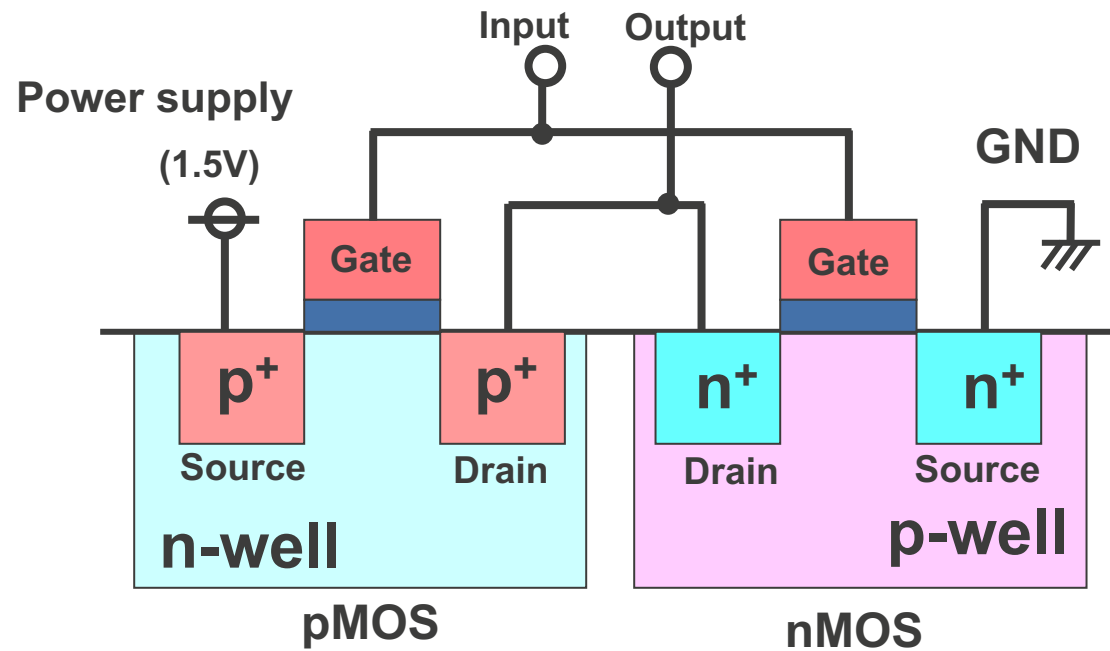

=



 


Simplest logic circuit with a pair of pMOS and nMOS transistors


Logic Circuit on Silicon Chip

Inverter


<Circuit Schematics>

   

<Cell Symbol>

 


<Layout pattern>

 


Inverter characteristics are defined by current characteristics of both transistors.

Logic Gate

 
- 2 input NAND ($O = \overline{A \cdot B}$)



- 2 input NOR ($O = \overline{A + B}$)

 

 
- Combinational gate ($O = \overline{A \cdot B + C}$)



- With **complementary** transistor configurations, all logic circuits can be implemented.
- Basically their complementary operations are similar to those of an inverter.

Flip Flops

Principle of operation

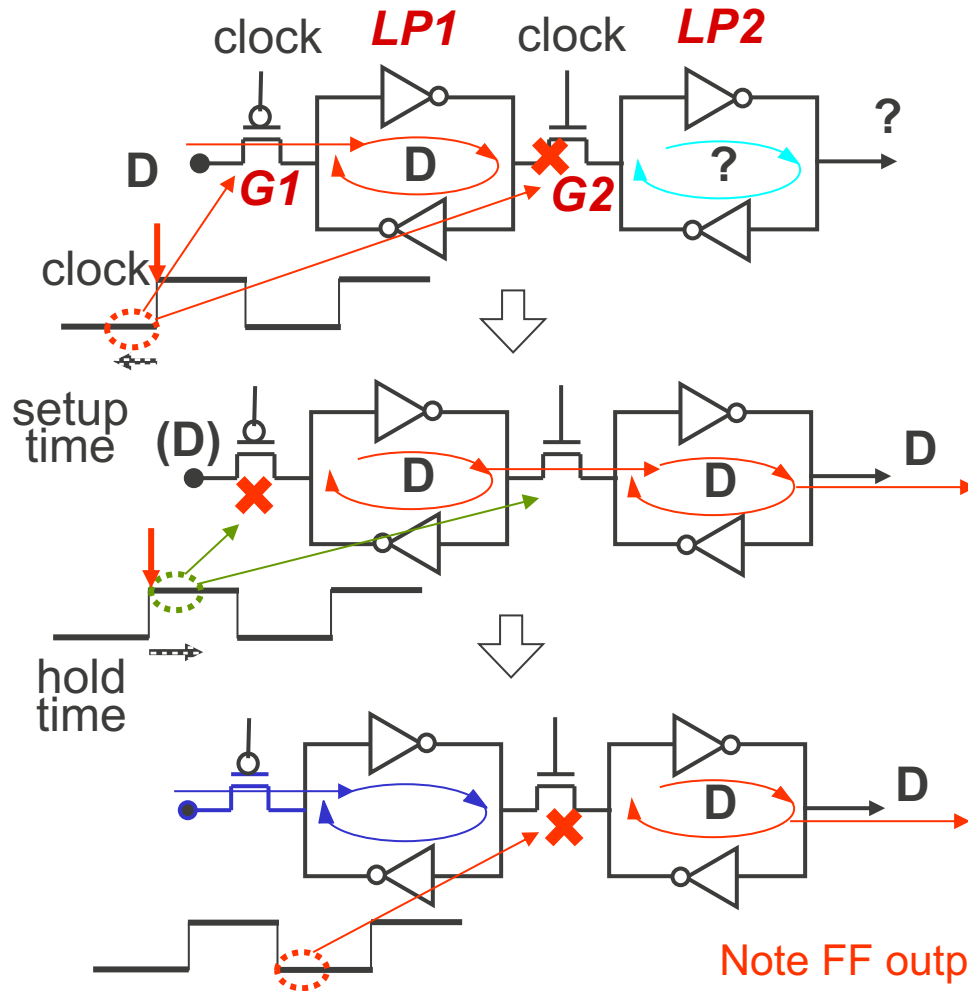

1. Gate G1 is ON while clock remains low, and data D is taken into loop LP1.

2. When clock rises, G1 is OFF and G2 is ON to pass data D into next loop LP2.


3. When clock goes low, G2 is OFF and LP2 keeps its data D.

Note FF output is not determined until any value is set from outside from logic simulation standpoint. Especially cares should be taken after power on.

Flip Flops

Metastable State (Metastability)

 - To set logical threshold voltage (V_{LT}) of each GATE at the same level is important to secure noise margin: $V_{LT} = 1/2 V_{DD}$.
- But big problem in FLIP FLOPs.




- When input V_{IN} is held at V_{LT} and then gate becomes OFF, the flip flop MIGHT may keep this level for unpredictable period.
- But actually when small plus noise is applied to left node of loop, V_{OUT} accordingly becomes 0. In minus case, V_{out} goes to 1.
- Behavior of V_{OUT} is **not predictable** depending upon noise level: **metastable**.

< hypothetical case >

Flip Flops



Metastable State (Metastability)

< actual case >

 

When falling edge of IN and rising edge of CLK are very close, voltages at inverter loop within FF become close to V_{LT} depending on timing of IN.


Succeeding behavior is unpredictable.

  

➡ This phenomenon surely happens when IN is asynchronous with CLK. OUT must be sensed at least one clock cycle after CLK rising edge under focusing.

SoC Design and Jigsaw Puzzle

 - **Jigsaw puzzle:**
assemble whole picture from many of interlocking pieces.
- **SoC design:**
assemble whole chip from components (cells) in circuits libraries, place and route them, so that they function harmoniously.



1. **Logic Cell library**
2. **Memory library**
3. **Analog Circuit library**

Circuit libraries on SoC

1. Logic cell library

- Primitive cells (Inverter, Buffer, NAND, NOR, FF, etc.)
- Data Path (Execution unit, selector, multiple-bit width)
- Clock Buffer
- Power Control Circuits (Power Switch, Substrate Bias Controller)

2. Memory library

- Register File
- RAM (Random Access Memory)
- ROM (Read Only Memory)

3. Analog Circuit library

- IO (Input and Output Buffer, Level Shifter)
- PLL (Phased Locked Loop)
- ADC (Analog to Digital Converter)
- RF (Radio Frequency Circuit)
- PA (Power Amplifier)

2.3 Electronic Signal Propagation on Silicon

Ideal wiring

Resistance(R) = 0


No signal attenuation.

Capacitance(C) = 0


Voltage can change at once

Reactance(L) = 0

Electric current can change at once

 

The ideal wire

 

Actual wiring on the silicon

$R \neq 0$

Voltage drops with current.


Power consumption.

$C \neq 0$

Voltage cannot jump up or down





$L \neq 0$

Current cannot jump up or down.

 

Circuit model

Effect of R, C and L

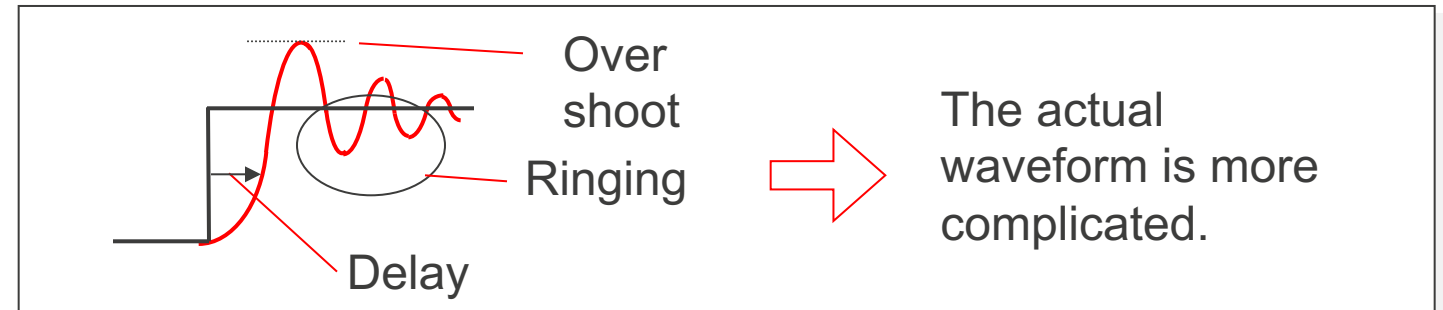   

Delay definitions

Logic delay through a gate is conveniently described by the propagation delay time, t_p . This is average time needed for the output to respond to a change in the input logic state:

$$t_p = \frac{1}{2} (t_{pHL} + t_{pLH})$$

Falling propagation delay (t_{pHL}):

Time for output to fall by 50% of V_{DD} references to input changes by 50% of V_{DD} .

Rising propagation delay (t_{pLH}):


Time for output to rise by 50% of V_{DD} references to input changes by 50% of V_{DD}

Fall time (t_f):

Time for output to fall from logical level “1” to level “0”.

Rise time (t_r):


 
Time for output to rise from logical level “0” to level “1”.



Logical level:


- Level “0”: from V_{SS} to 10% of V_{DD} ;
- Level “1”: from 90% of V_{DD} to V_{DD} .

Charge up & Discharge

  

Rise time and fall time: times required to charge or discharge the load capacitor.
Large load capacitance results in large delay.

Rise time - Delay of charge up

 

Note: Assume at initial state, C_L was fully dis-charged to 0V

◆ Current flows when pMOS is ON,

$$I_s = |I_{ds}| \\ = (\beta_p/2) \cdot (V_{DD} - |V_{thp}|)^2$$

◆ Electric charge to be charged


$$Q = C_L \cdot V_{DD}$$



Rise time is:

$$t_r = Q/|I_{ds}| \\ = \frac{C_L \cdot V_{DD}}{(\beta_p/2) \cdot (V_{DD} - |V_{thp}|)^2}$$

Fall time - Delay for discharge

 

Note: Assume at initial state, C_L was fully charged to V_{DD}

◆ Current flows when nMOS is ON,

$$I_{ds} = (\beta_n/2) \cdot (V_{DD} - V_{thn})^2$$

◆ Electric charge to be discharged

$$Q = C_L \cdot V_{DD}$$



Fall time is:

$$t_f = Q/I_{ds}$$

$$= \frac{C_L \cdot V_{DD}}{(\beta_n/2) \cdot (V_{DD} - V_{thn})^2}$$




Summary of delay time

$$\text{Delay time} = \begin{cases} \frac{C_L \cdot V_{DD}}{(\beta_p/2) \cdot (V_{DD} - |V_{thp}|)^2} & \text{: rise time} \\ \frac{C_L \cdot V_{DD}}{(\beta_n/2) \cdot (V_{DD} - V_{thn})^2} & \text{: fall time} \end{cases}$$

$$\beta = \underset{\substack{\uparrow \\ \text{Mobility}}}{\mu} \cdot \underset{\substack{\uparrow \\ \text{Capacity of gate oxide per} \\ \text{unit area}}}{C_{ox}} \cdot W/L \quad \Rightarrow \quad \begin{cases} \blacklozenge \text{ Faster, if gate length } L \text{ is shorter} \\ \blacklozenge \text{ Faster, if gate width } W \text{ is wider} \end{cases}$$

2.4 Problem with Electronic Signal


Gate Delay & Wiring Delay

   

Countermeasures for reducing delay

- Reduction of the resistance
- Reduction of the capacitance
- Larger driving force



Skew

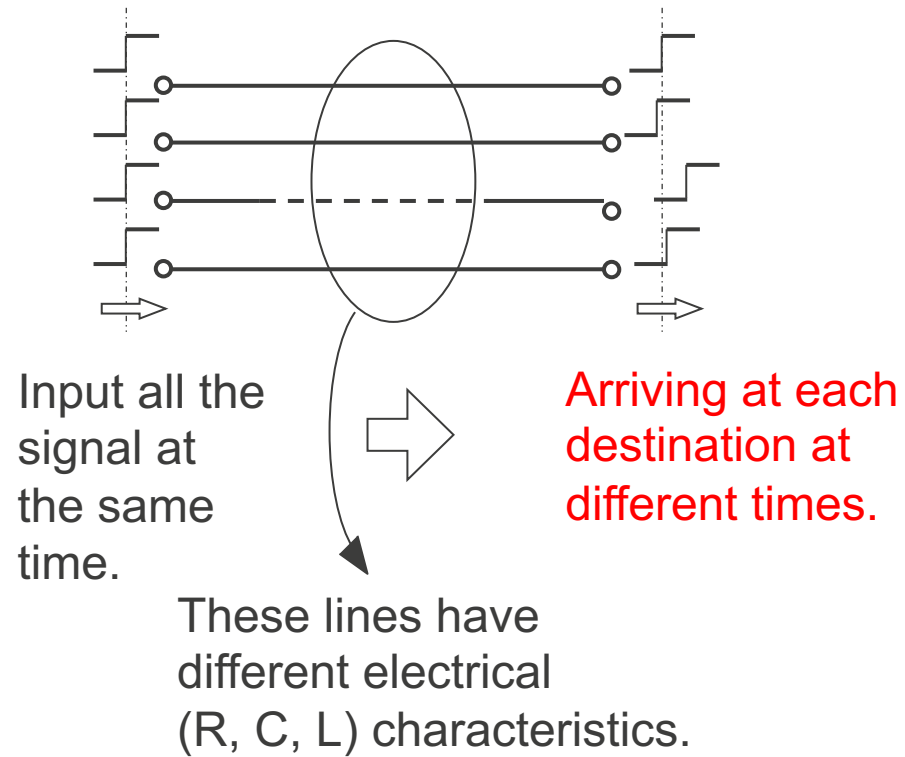

skew

For more-than-1-bit signal, skew is always a big problem.

 
 
Clock signal will always suffer from skew problem.



Skew causes difficulty in wiring clock lines, especially in higher frequency range and limits the clock speed.


Hazard & Glitch

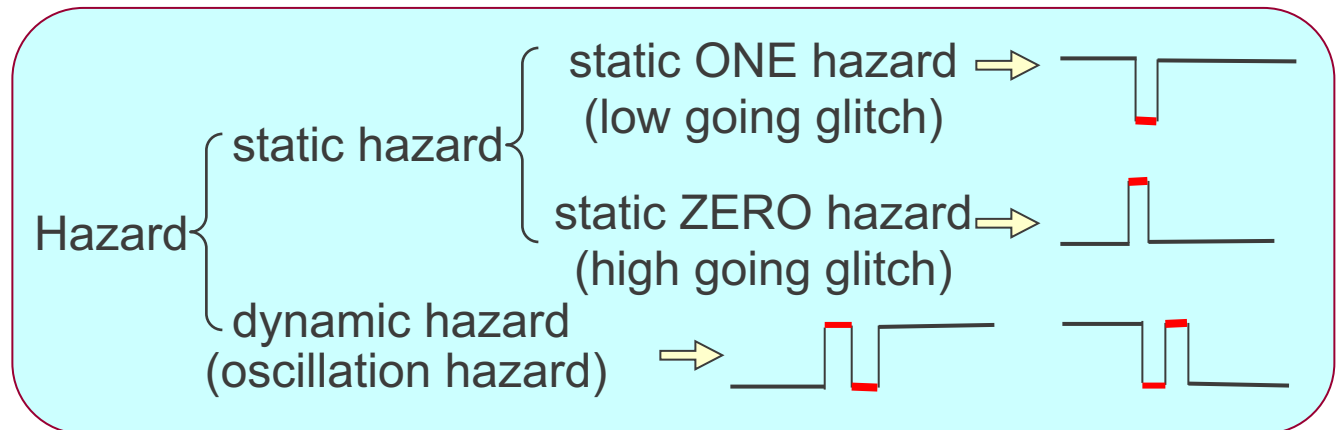 Hazard is a problem caused by a small timing difference among several signals.





How to avoid hazard?

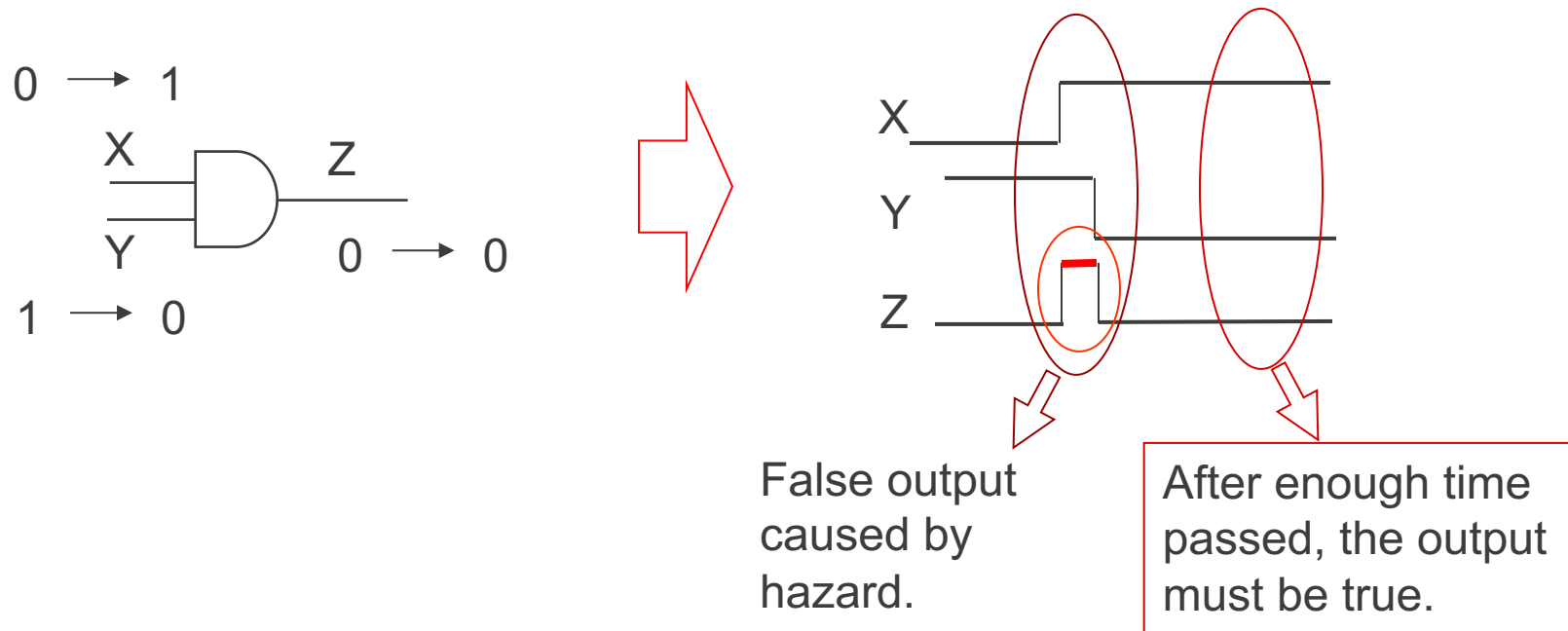It is difficult to prevent hazard. However, we can avoid using hazard signal by selecting a timing to use the signal.



To avoid hazard, outputs of combinational logic must be used after proper time period passed since input signals become stable.

  
When handling edge signal, you must be very careful about hazard, because edge signal is very sensitive to hazard. Especially, clock signal is very sensitive to hazard.



Hazard cause big problems resulting in malfunction of a system. Synchronous design may help us to get out of these problems.

To avoid hazard on clock signal, do not insert any combinational logic in clock line.

Power Consumption

 


$$\begin{aligned}\text{Electric power} &\sim V.I \sim V.Q/T \sim V.CV/T \\ &\sim C.V^2/T \\ &\sim f.C.V^2\end{aligned}$$

The power consumption of CMOS

$$P \sim f.C.V^2$$

Dynamic power

 

The keys to reduce power consumption.




- <1> Making operation voltage low
- <2> Lowering an operating frequency.
- <3> Reducing capacitance and so on.



Power consumption limits the operating speed.
Large power consumption makes it difficult to design packages.


However, the **leakage current is becoming significant**, we have to apply partial power off strategy to reduce power significantly.

Short Circuit Power

   

Power consumption by short circuit current is about less than 10 to 15% of the total power consumption

Leak Current

 

Devices with large leak current are not applicable to battery powered products.

Gate size shrink and low voltage operation



Thinner gate insulator



The increase of the gate leak by the tunnel current




Counter measure




High K material
Partial power-off

 dielectric constant,
or electric permittivity





Metastability of Flip-Flop

 


If **In** is given a value, such as mean value of low and high voltage, **Out** becomes unstable for some period and we can not tell what the final value shall be.

→ This is called “**metastability**”.

 
 


→ We cannot predict the result.

 

This may happen when input signal changes at the instant of the clock pulse.

 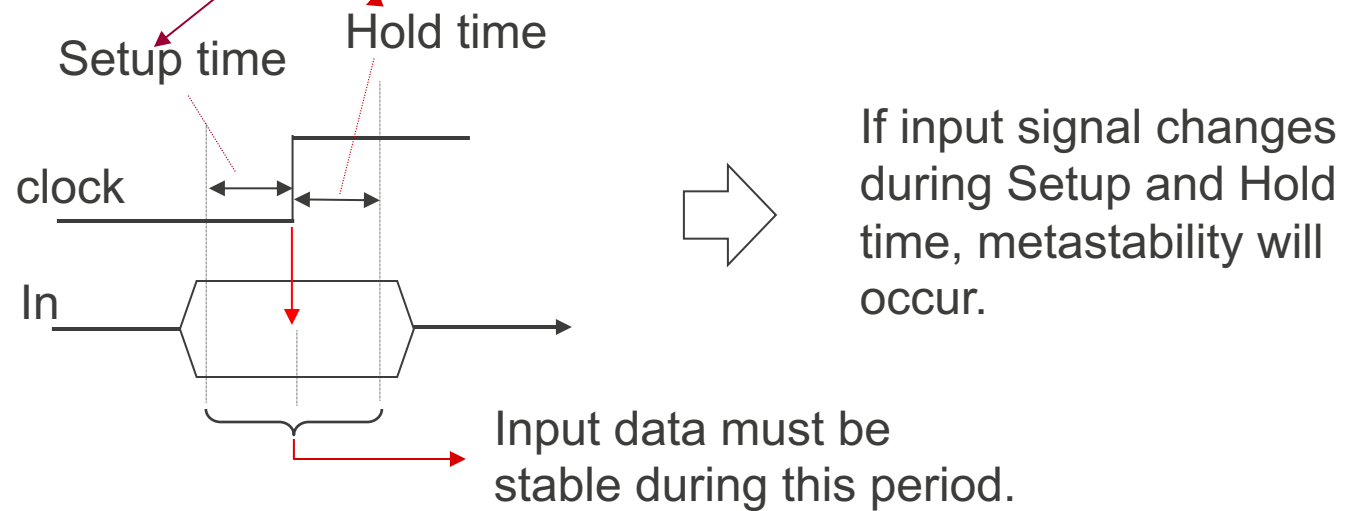In many cases, metastability can be avoided by ensuring that inputs are held constant for specified periods **before** and **after** the clock pulse.



In synchronous design, by applying STA, we can avoid metastability of FFs.

Typical Setup time or Hold time is less than 100 p sec.

Unknown initial value of Flip-Flop

We can not tell the value of FF right after power on. (How about SRAM?)

→ The output signal of FFs must be used after proper initialization sequence.



Many problems caused by unknown initial value of FF have been experienced. **Pay special attention to this issue whenever you use FFs (or SRAM).**



If a logic you designed uses the unknown initial values of FFs in a way that they cause unexpected operation, it means you have implemented a logic bug.

Fan-out



Because of output voltage drop, there is a limitation (fan-out) in the number of the circuits which can be connected to an output.



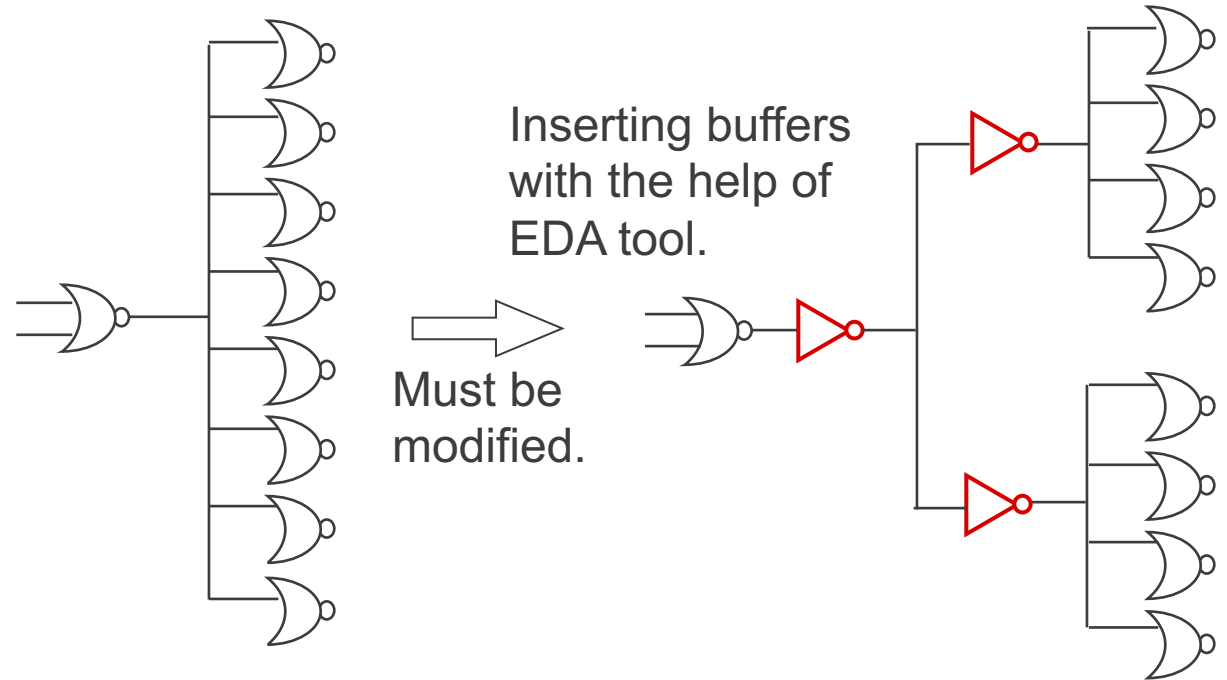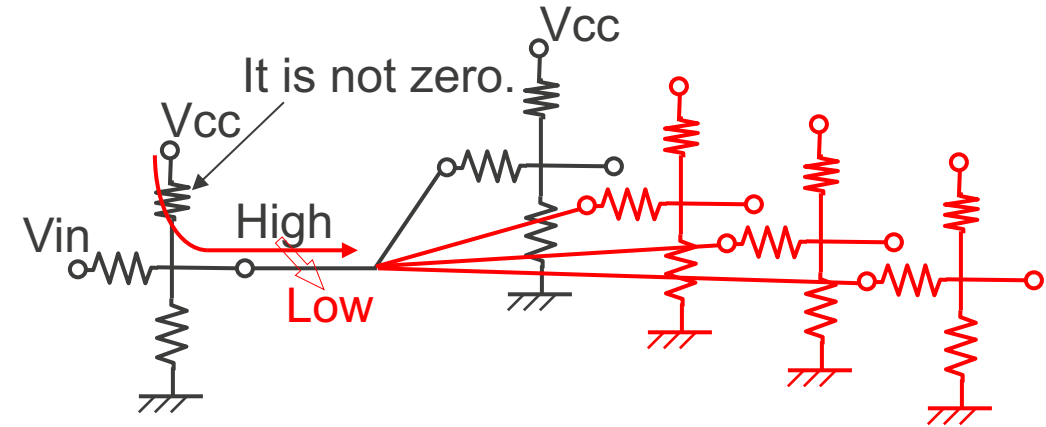Fan-out problem causes malfunction of the circuits. EDA tools can help us to avoid this problem.




 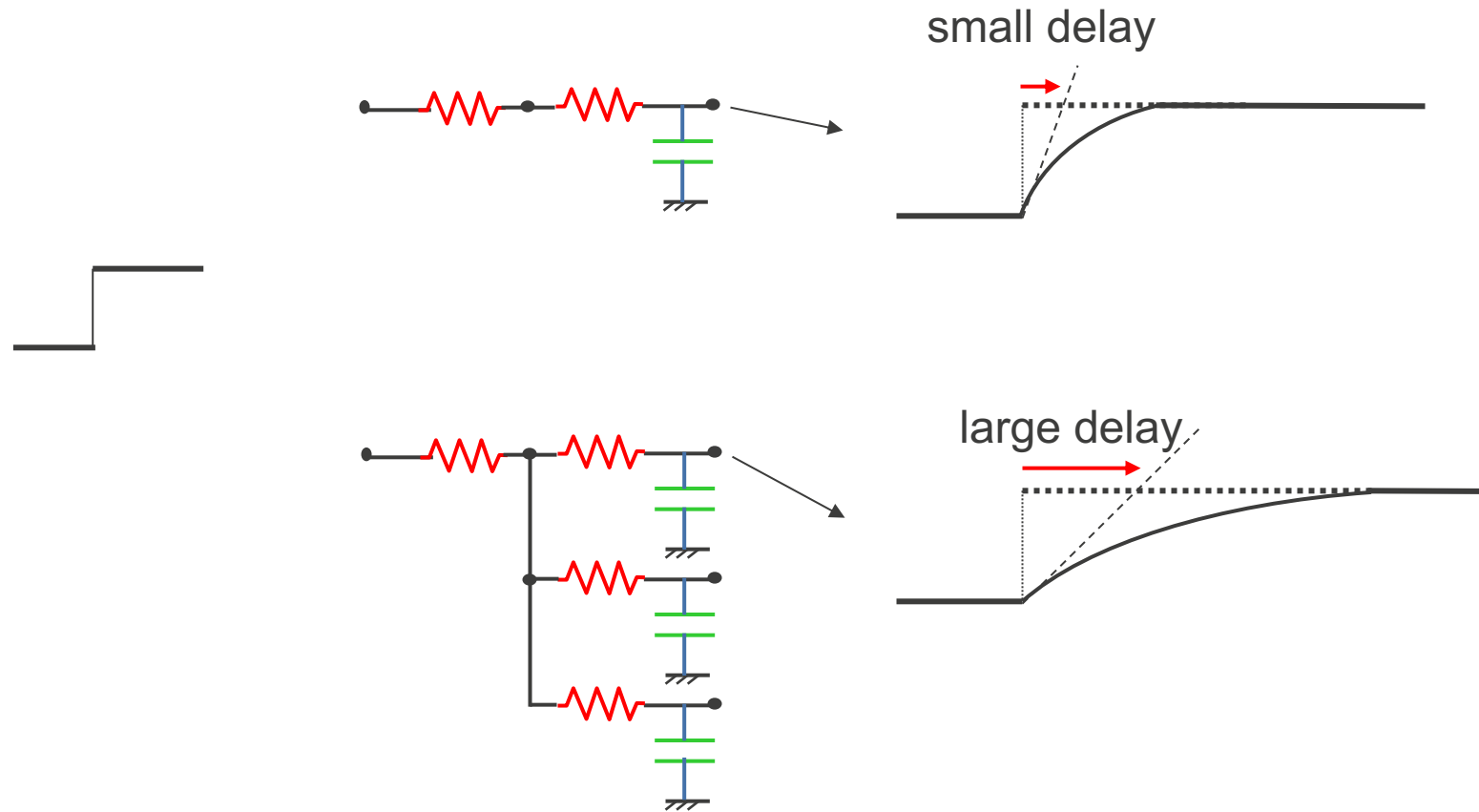Because larger load result in larger delay as shown below, fan out issue is also related to speed.




Sometimes delay of N stage gate logic is larger than that of having more stages gate logic if some gates have larger load.

Ground bounce

 


Cannot keep the potential of the ground at zero when there is a large current in the neighborhood.

Sharing the ground with other signals

 

 A false signal can be observed when the potential of the ground is shaken by the other signal.





Ground bounce

Simultaneous signal change and ground bounce




Ground bounce creates false signal on certain signal line, thus sometimes causes a malfunction of a device.

Cross talk

 
 


 Cross talk creates false signal on certain signal line, thus sometimes causes a malfunction of a device.



IR drop creates insufficient power supply to certain circuit on silicon and limit miniaturization and operating frequency.



EMC/EMI

 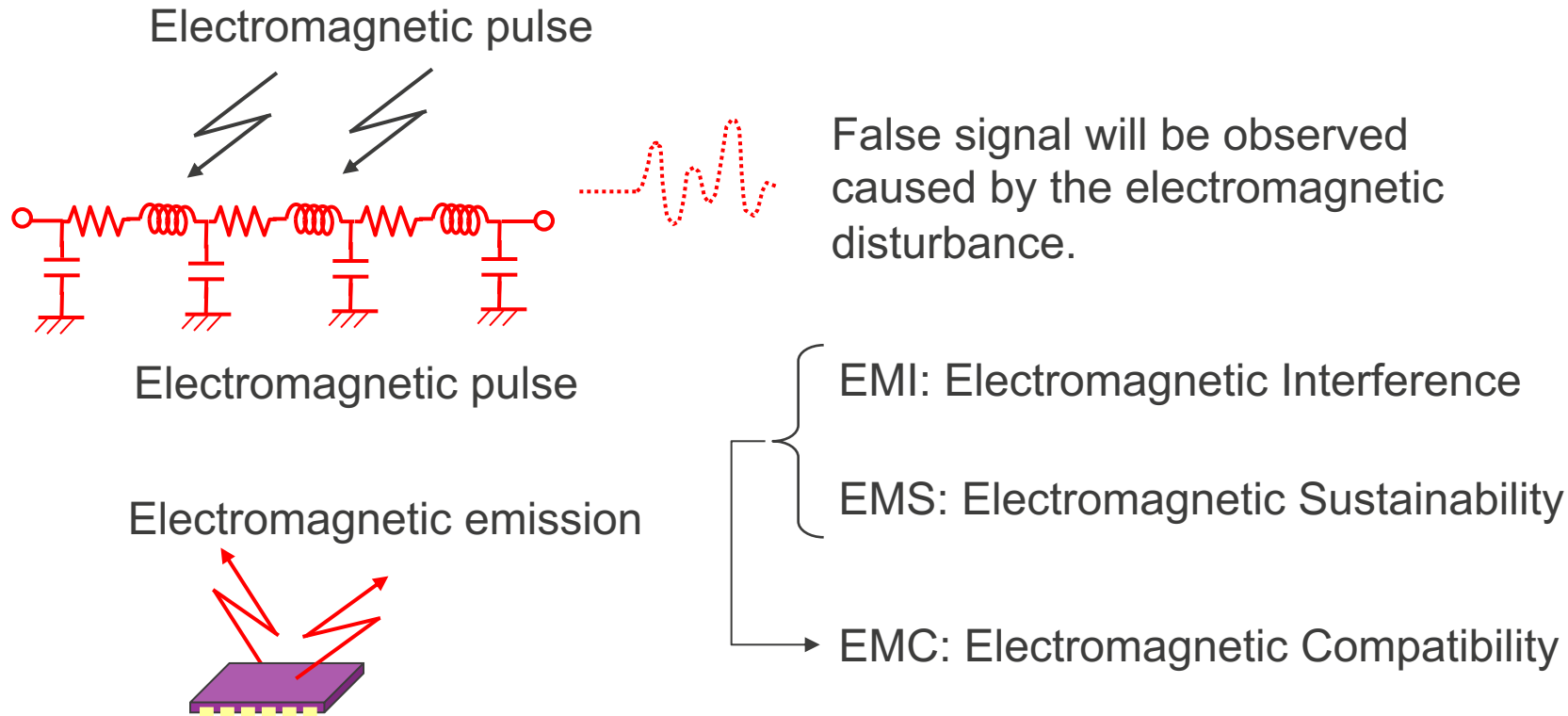

Electromagnetic interference may creates false signal on certain signal line, thus sometimes causes a malfunction of a device. It becomes difficult to comply with EMC guide lines as operating frequency of devices goes high.



Radiation from the package and cosmic ray

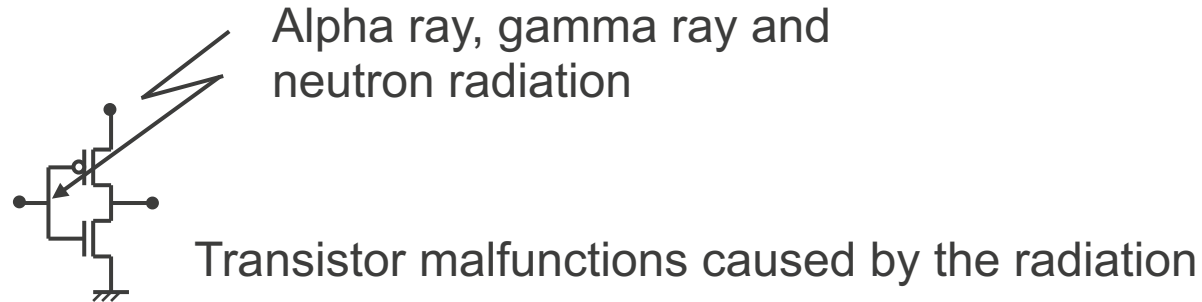 The influence of neutron radiation and so on, are becoming significant.




Large scale memory can not avoid this problem, therefore some error correction system is necessary for such large scale memory.

 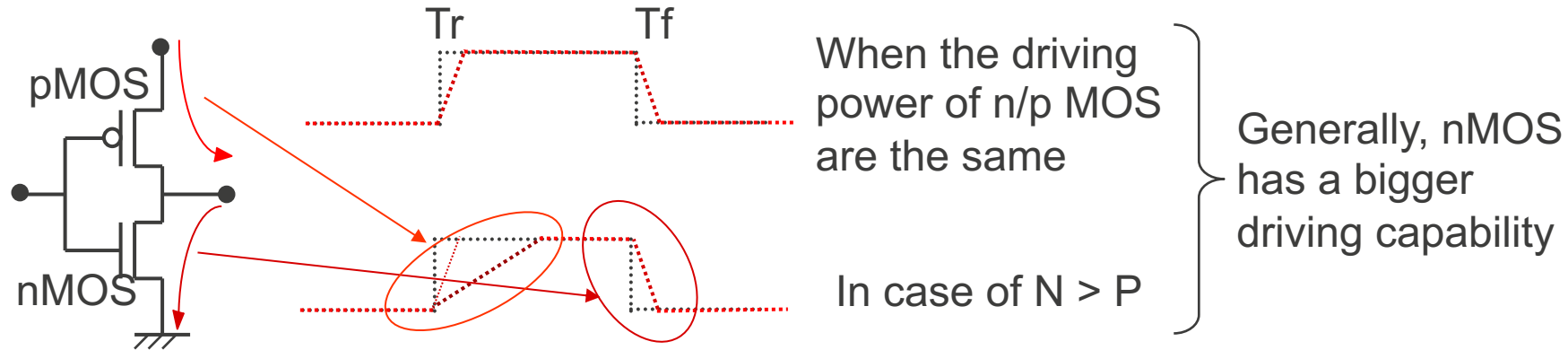The different characteristic of nMOS & pMOS



The rising becomes gentle because the driving power of pMOS is weak.

 
It becomes difficult to keep the duty ratio of on/off such as the clock at 50%.



Clock skew problem may become critical when inserting a buffer into the clock line.



Electron migration

 Atoms of wire material, aluminum or copper, are kicked out of the wire line by electrons. This sometimes causes a breaking of wire.



Some DA tool can give us warning that there may be electron migration problem.

Other issues

 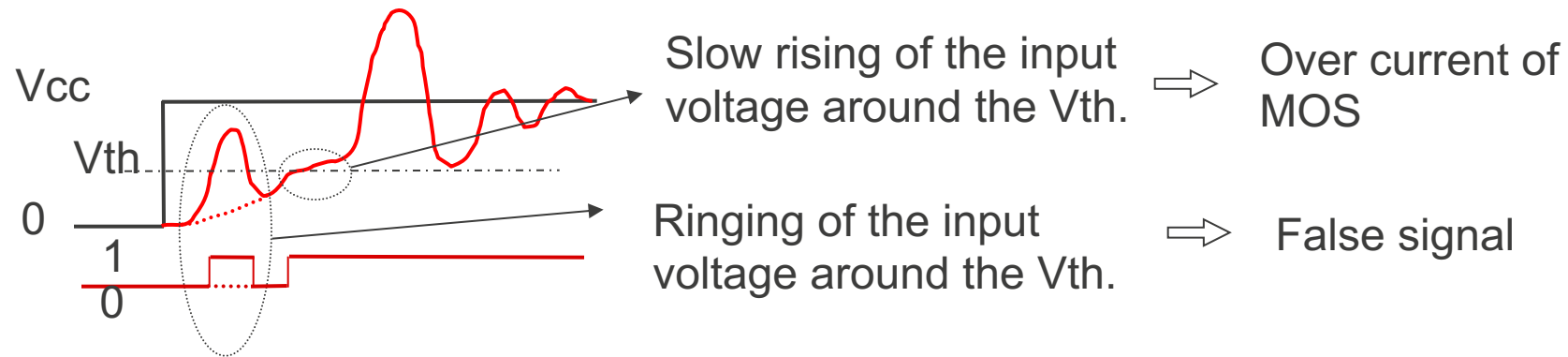

[Renesas.com](https://www.renesas.com)